



Verilog HDL

Design Examples

1. Digital system designs and practices: Using Verilog HDL and FPGAs
2. Fundamentals of Digital Logic with Verilog Design 3e

Teacher: Prof. Shu-Yen Lin

Email: sylin@saturn.yzu.edu.tw

Date: 2020/11/11

Outline

Combinational Logic Modules

- Decoders
- Encoders
- Multiplexers
- Demultiplexers

Sequential Logic Modules


- Flip-flops
- Memory elements
- Data Registers
- Counters
- Finite State Machines (FSM)

Combinational Logic Modules


- Decoders
- Encoders
- Multiplexers
- Demultiplexers

Decoder Block Diagrams

❖ n -to- m decoders

 


(a) Noninverted output

 


(b) Inverted output

A 2-to-4 Decoder Example

 

| E | x_1 | x_0 | Y_3 | Y_2 | Y_1 | Y_0 |
|-----|--------|--------|-------|-------|-------|-------|
| 1 | ϕ | ϕ | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 | 1 |

(b) Function table

 

(c) Logic circuit

A 2-to-4 Decoder Example

// a 2-to-4 decoder with active low output

always @(x or enable_n)

if (enable_n) y = 4'b1111; else

case (x)


2'b00 : y = 4'b1110;

2'b01 : y = 4'b1101;

2'b10 : y = 4'b1011;

2'b11 : y = 4'b0111;

endcase

 

A 2-to-4 Decoder with Enable Control

// a 2-to-4 decoder with active-high output

always @(x or enable)

if (!enable) y = 4'b0000; else

case (x)


2'b00 : y = 4'b0001;

2'b01 : y = 4'b0010;

2'b10 : y = 4'b0100;


2'b11 : y = 4'b1000;

endcase

 


Encoder Block Diagrams

❖ m -to- n encoders

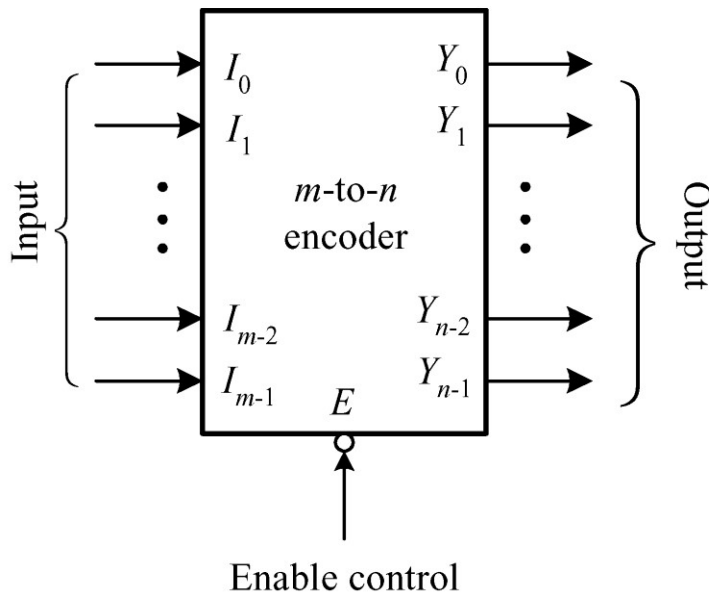

(a) Noninverted output

 


(b) Inverted output

A 4-to-2 Encoder Example

| I_3 | I_2 | I_1 | I_0 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |

(a) Function table

 

(b) Logic circuit

A 4-to-2 Encoder Example

// a 4-to-2 encoder using if ... else structure

always @(in) begin

if (in == 4'b0001) y = 0; else


if (in == 4'b0010) y = 1; else

if (in == 4'b0100) y = 2; else

if (in == 4'b1000) y = 3; else

y = 2'bx;

end

 

Another 4-to-2 Encoder Example

// a 4-to-2 encoder using case structure

always @(in)

case (in)

4'b0001 : y = 0;


4'b0010 : y = 1;

4'b0100 : y = 2;


4'b1000 : y = 3;

default : y = 2'bx;

endcase

 

A 4-to-2 Priority Encoder

 

(a) Block diagram

| Input | | | | Output | |
|-------|--------|--------|--------|--------|-------|
| I_3 | I_2 | I_1 | I_0 | A_1 | A_0 |
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | ϕ | 0 | 1 |
| 0 | 1 | ϕ | ϕ | 1 | 0 |
| 1 | ϕ | ϕ | ϕ | 1 | 1 |

(b) Function table

A 4-to-2 Priority Encoder Example

// using if ... else structure

assign valid_in = |in;

always @(in) begin

if (in[3]) y = 3; else


if (in[2]) y = 2; else

if (in[1]) y = 1; else

if (in[0]) y = 0; else


y = 2'bx;

end

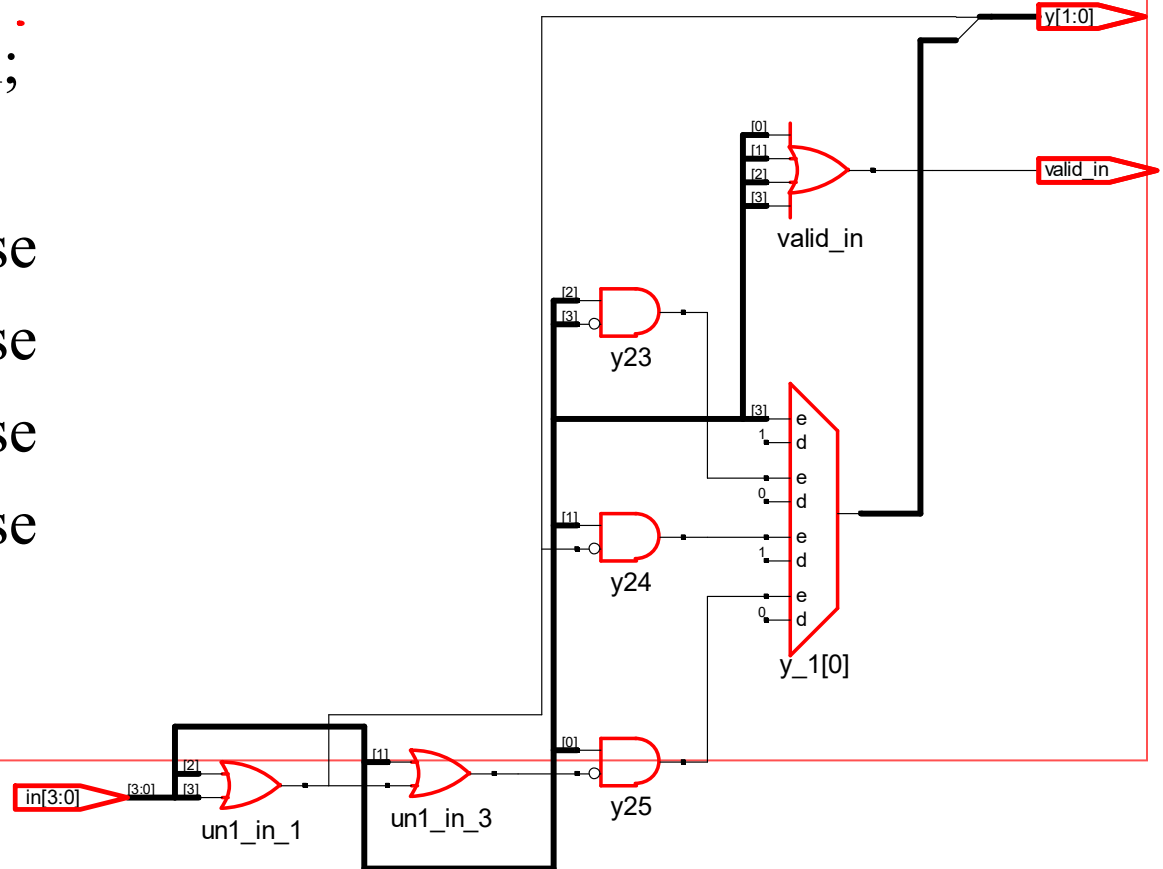


Another 4-to-2 Priority Encoder Example

```
// using casex structure
assign valid_in = |in;
always @(in) casex (in)
  4'b1xxx: y = 3;
  4'b01xx: y = 2;
  4'b001x: y = 1;
  4'b0001: y = 0;
  default: y = 2'bx;
endcase
```

 


Multiplexer Block Diagrams

❖ m -to-1 ($m = 2^n$) multiplexers

 


(a) Without enable control

 

(b) With enable control

A 4-to-1 Multiplexer Example


❖ Gate-based 4-to-1 multiplexers

 

(a) Logic symbol

| S_1 | S_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

(b) Function table

 

(c) Logic circuit

An n -bit 4-to-1 Multiplexer Example

// an N-bit 4-to-1 multiplexer using conditional operator

parameter N = 4; //

input [1:0] select;


input [N-1:0] in3, in2, in1, in0;

output [N-1:0] y;

assign y = select[1] ?

(select[0] ? in3 : in2) :

(select[0] ? in1 : in0) ;

 

The Second n -bit 4-to-1 Multiplexer Example

```
// an N-bit 4-to-1 multiplexer with enable control
parameter N = 4;
input [1:0] select;
input enable;
input [N-1:0] in3, in2, in1, in0;
output reg [N-1:0] y;

always @(select or enable or in0 or in1 or in2 or in3)
    if (!enable) y = {N{1'b0}};
    else y = select[1] ?
        (select[0] ? in3 : in2) :
        (select[0] ? in1 : in0);
```

The Third n -bit 4-to-1 Multiplexer Example

// an N-bit 4-to-1 multiplexer using case structure

parameter N = 8;

input [1:0] select;

input [N-1:0] in3, in2, in1, in0;

output reg [N-1:0] y;

always @(*)

case (select)


2'b11: y = in3 ;

2'b10: y = in2 ;

2'b01: y = in1 ;


2'b00: y = in0 ;

endcase

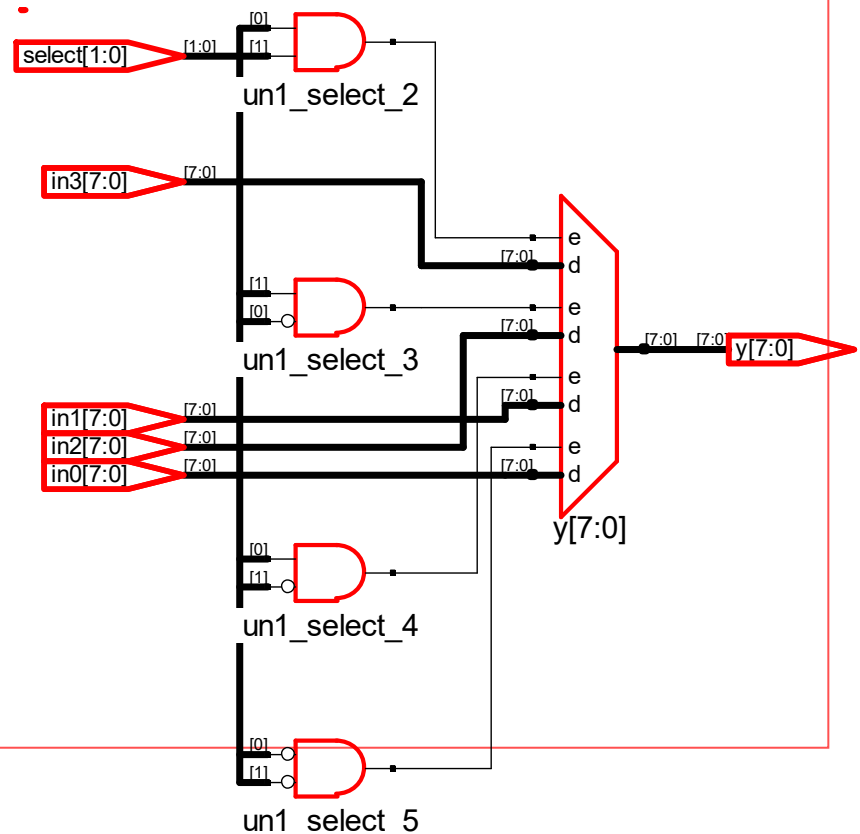


DeMultiplexer Block Diagrams

❖ 1-to- m ($m = 2^n$) demultiplexers

 


(a) Without enable control

 

(b) With enable control

A 1-to-4 DeMultiplexer Example


❖ Gate-based 1-to-4 demultiplexers

 

(a) Logic symbol

| E | S_1 | S_0 | Y_3 | Y_2 | Y_1 | Y_0 |
|-----|--------|--------|-------|-------|-------|-------|
| 1 | ϕ | ϕ | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | D |
| 0 | 0 | 1 | 0 | 0 | D | 0 |
| 0 | 1 | 0 | 0 | D | 0 | 0 |
| 0 | 1 | 1 | D | 0 | 0 | 0 |

(b) Function table

 

(c) Logic circuit

An n -bit 1-to-4 DeMultiplexer Example

```
// an N-bit 1-to-4 demultiplexer using if ... else structure
```

```
parameter N = 4; // default width
```

```
input    [1:0] select;
```

```
input    [N-1:0] in;
```

```
output reg [N-1:0] y3, y2, y1, y0;
```

```
always @(select or in) begin
```


```
    if (select == 3) y3 = in; else y3 = {N{1'b0}};
```

```
    if (select == 2) y2 = in; else y2 = {N{1'b0}};
```

```
    if (select == 1) y1 = in; else y1 = {N{1'b0}};
```

```
    if (select == 0) y0 = in; else y0 = {N{1'b0}};
```

```
end
```

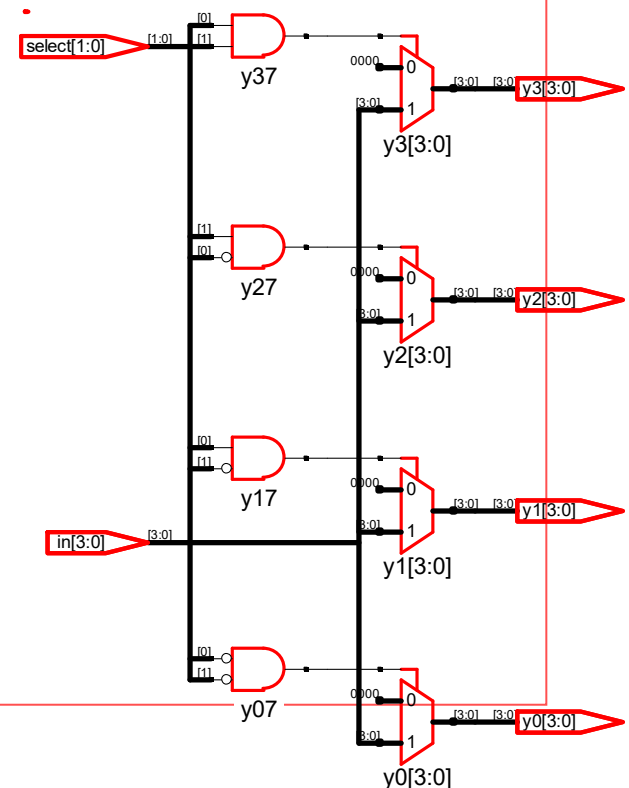

The Second n -bit 1-to-4 DeMultiplexer Example

```
// an N-bit 1-to-4 demultiplexer with enable control
parameter N = 4;    // Default width
...
output reg [N-1:0] y3, y2, y1, y0;
always @(select or in or enable) begin
    if (enable)begin
        if (select == 3) y3 = in; else y3 = {N{1'b0}};
        if (select == 2) y2 = in; else y2 = {N{1'b0}};
        if (select == 1) y1 = in; else y1 = {N{1'b0}};
        if (select == 0) y0 = in; else y0 = {N{1'b0}};
    end else begin
        y3 = {N{1'b0}}; y2 = {N{1'b0}}; y1 = {N{1'b0}}; y0 = {N{1'b0}}; end
    end
```

Sequential Logic Modules

- Flip-flops
- Data Registers
- Shift registers
- Counters

Asynchronous Reset *D*-Type Flip-Flops

```
// asynchronous reset D-type flip-flop
module DFF_async_reset (clk, reset_n, d, q);
...
output reg q;

always @(posedge clk or negedge reset_n)
    if (!reset_n) q <= 0;
    else          q <= d;
```

Synchronous Reset *D*-Type Flip-Flops


```
// synchronous reset D-type flip-flop
module DFF_sync_reset (clk, reset, d, q);
...
output reg q;

always @(posedge clk)
    if (reset) q <= 0;
    else      q <= d;
```

D-type latch

```
module latch (D, clk, Q);  
  input D, clk;  
  output reg Q;  
  
  always @(D, clk)  
    if (clk)  
      Q = D;  
  
endmodule
```

Data Registers

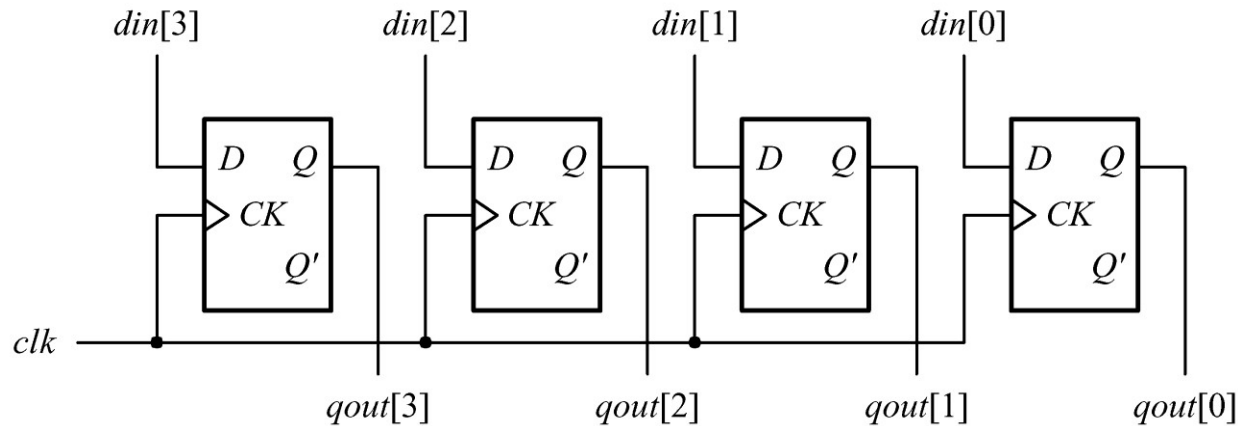

// an n-bit data register

```
module register(clk, din, qout);
```

```
parameter N = 4; // number of bits
```

```
...
```

```
input  [N-1:0] din;
```

```
output reg [N-1:0] qout;
```

```
always @(posedge clk) qout <= din;
```

Data Registers


```
// an n-bit data register with asynchronous reset
module register_reset (clk, reset_n, din, qout);
parameter N = 4; // number of bits
...
input  [N-1:0] din;
output reg [N-1:0] qout;
always @(posedge clk or negedge reset_n)
    if (!reset_n) qout <= {N{1'b0}};
    else          qout <= din;
```

Data Registers


```
// an N-bit data register with synchronous load and
// asynchronous reset
parameter N = 4; // number of bits
input  clk, load, reset_n;
input  [N-1:0] din;
output reg [N-1:0] qout;

always @(posedge clk or negedge reset_n)
    if (!reset_n)  qout <= {N{1'b0}};
    else if (load) qout <= din;
```

Shift Registers

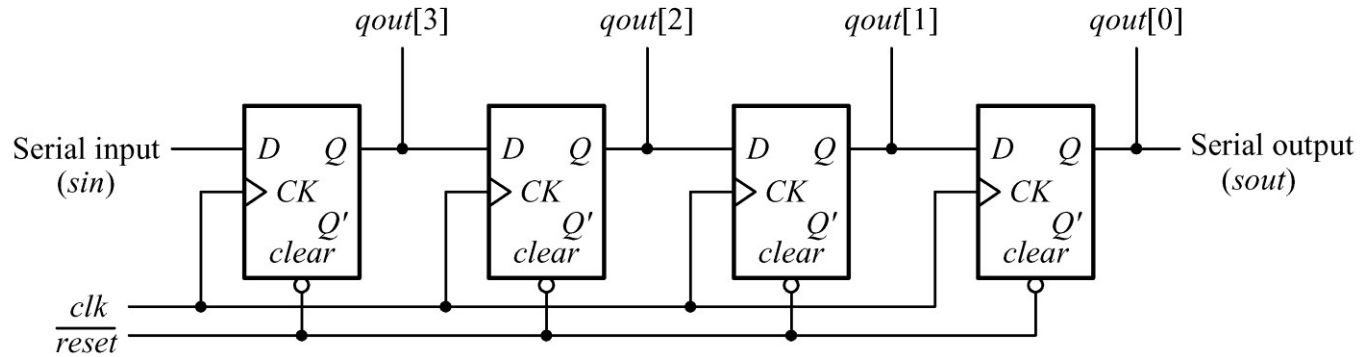

(a) Logic circuit

 


(b) Timing

Shift Registers


```
// a shift register module example
module shift_register(clk, reset_n, din, qout);
Parameter N = 4; // number of bits
....
output reg [N-1:0] qout;

always @(posedge clk or negedge reset_n)
    if (!reset_n) qout <= {N{1'b0}};
    else          qout <= {din, qout[N-1:1]};
```


Binary Ripple Counters

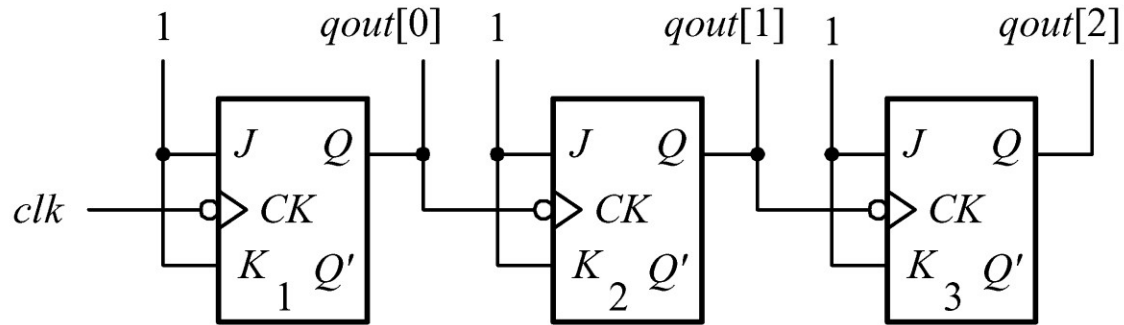

(a) Logic diagram

 

(b) Timing

Binary Ripple Counters

// a 3-bit ripple counter module example

```
module ripple_counter(clk, qout);
```

```
...
```

```
output reg [2:0] qout;
```

```
wire  c0, c1;
```

// the body of the 3-bit ripple counter

```
assign c0 = qout[0], c1 = qout[1];
```

```
always @(negedge clk)
```

```
    qout[0] <= ~qout[0];
```

```
always @(negedge c0)
```

```
    qout[1] <= ~qout[1];
```

```
always @(negedge c1)
```


```
    qout[2] <= ~qout[2];
```

Binary Ripple Counters

```
// a 3-bit ripple counter with enable control
module ripple_counter_enable(clk, enable, reset_n, qout);
...
output reg [2:0] qout;
wire c0, c1;
assign c0 = qout[0], c1 = qout[1];
always @(posedge clk or negedge reset_n)
    if (!reset_n) qout[0] <= 1'b0;
    else if (enable) qout[0] <= ~qout[0];
always @(posedge c0 or negedge reset_n)
    if (!reset_n) qout[1] <= 1'b0;
    else if (enable) qout[1] <= ~qout[1];
always @(posedge c1 or negedge reset_n)
    if (!reset_n) qout[2] <= 1'b0;
    else if (enable) qout[2] <= ~qout[2];
```

Finite State Machines (1)

 ❖ **Moore machine:** a finite-state machine whose output values are determined solely by its **current state**.



```
module moore (Clock, w, Resetn, z);
  input Clock, w, Resetn;
  output z;
  reg [1:0] y, Y;
  parameter A = 2'b00, B = 2'b01, C = 2'b10;


  always @(w, y)
  begin
    case (y)
      A: if (w == 0) Y = A;
         else Y = B;
      B: if (w == 0) Y = A;
         else Y = C;
      C: if (w == 0) Y = A;
         else Y = C;
      default: Y = 2'bxx;
    endcase
  end

  always @(posedge Clock, negedge Resetn)
  begin
    if (Resetn == 0)
      y <= A;
    else
      y <= Y;
    end

    assign z = (y == C);
  end
endmodule
```

Finite State Machines (2)

 ❖ **Mealy machine:** A finite-state machine whose output values are determined both by its **current state** and **the current inputs**.



```
module mealy (Clock, w, Resetn, z);
  input Clock, w, Resetn ;
  output reg z ;
  reg y, Y;
  parameter A = 1'b0, B = 1'b1;
```

```
  always @(w, y)
  case (y)
    A: if (w == 0)
      begin
        Y = A;
        z = 0;
      end
    else
      begin
        Y = B;
        z = 0;
      end
    B: if (w == 0)
      begin
        Y = A;
        z = 0;
      end
    else
      begin
        Y = B;
        z = 1;
      end
  endcase
```

```
  always @(posedge Clock , negedge Resetn)
  if (Resetn == 0)
    y <= A;
  else
    y <= Y;
```

```
endmodule
```